

CLOCK DOMAINS AND TIMING



AGENDA

- › Clock Domains
- › Timing/Synchronization Issues
- › FPGA Clock Generation & Distribution
- › Reset Circuits

CLOCK DOMAINS



↑ 8.1920 MHz


Tx Data




Rx Data



↑ 8.1921 MHz

 


CLOCK DOMAINS

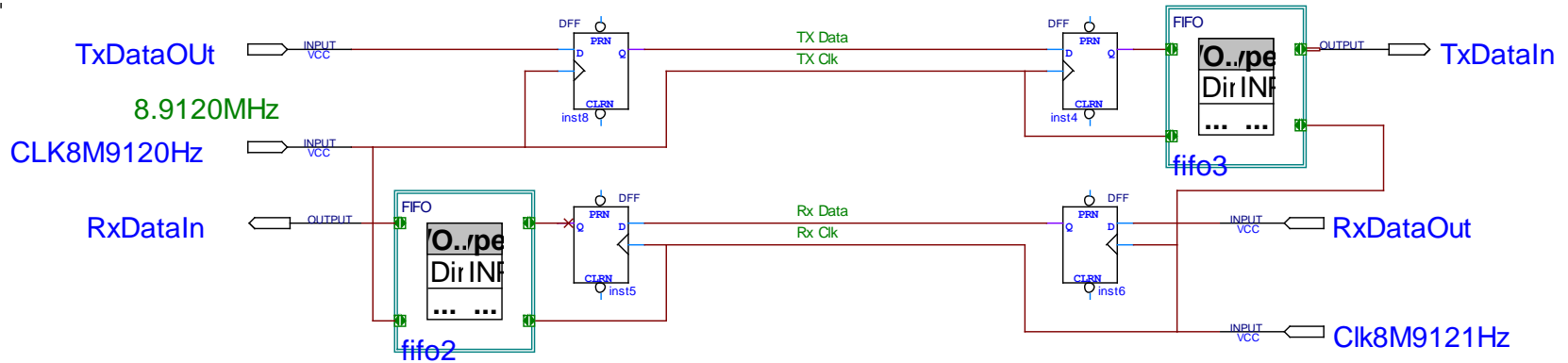

Solution:


- › Tx / Rx Data have companion clocks
- › Clock domain crossing in FIFO / Dual-Port Mem etc.

CLOCK DOMAIN DEFINITION

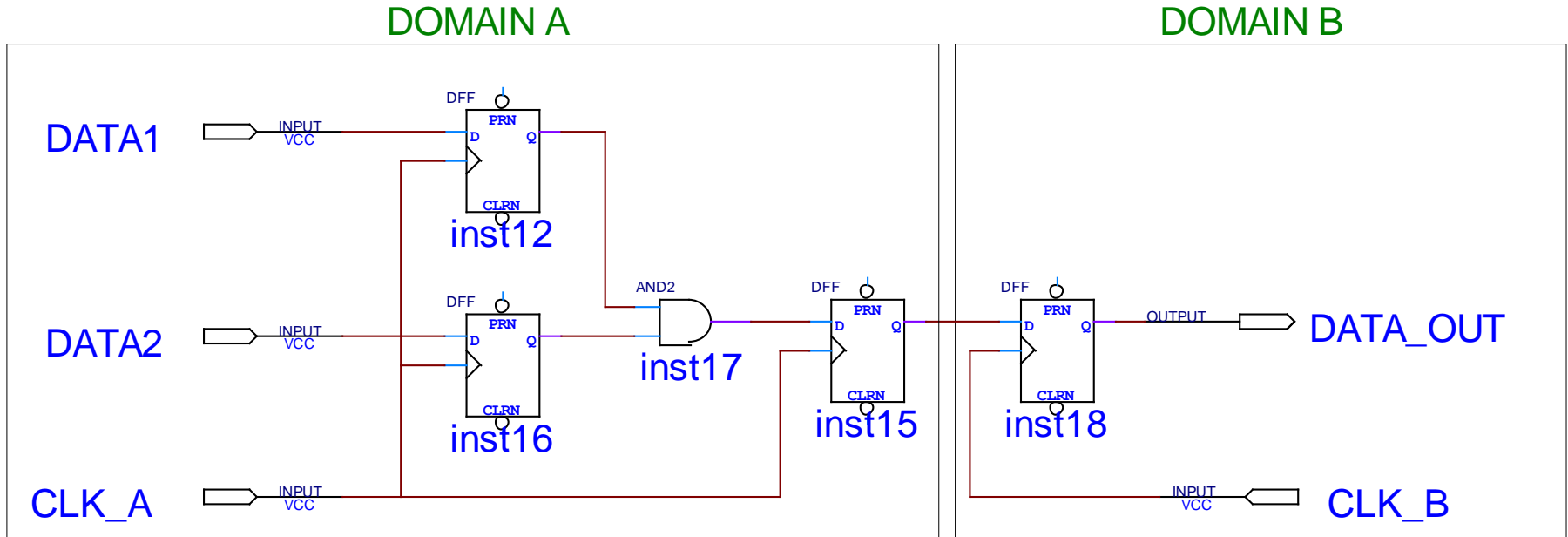



- › A Clock Domain is a section of logic where all synchronous elements are clocked by the same clock

CLOCK DOMAINS TYPES

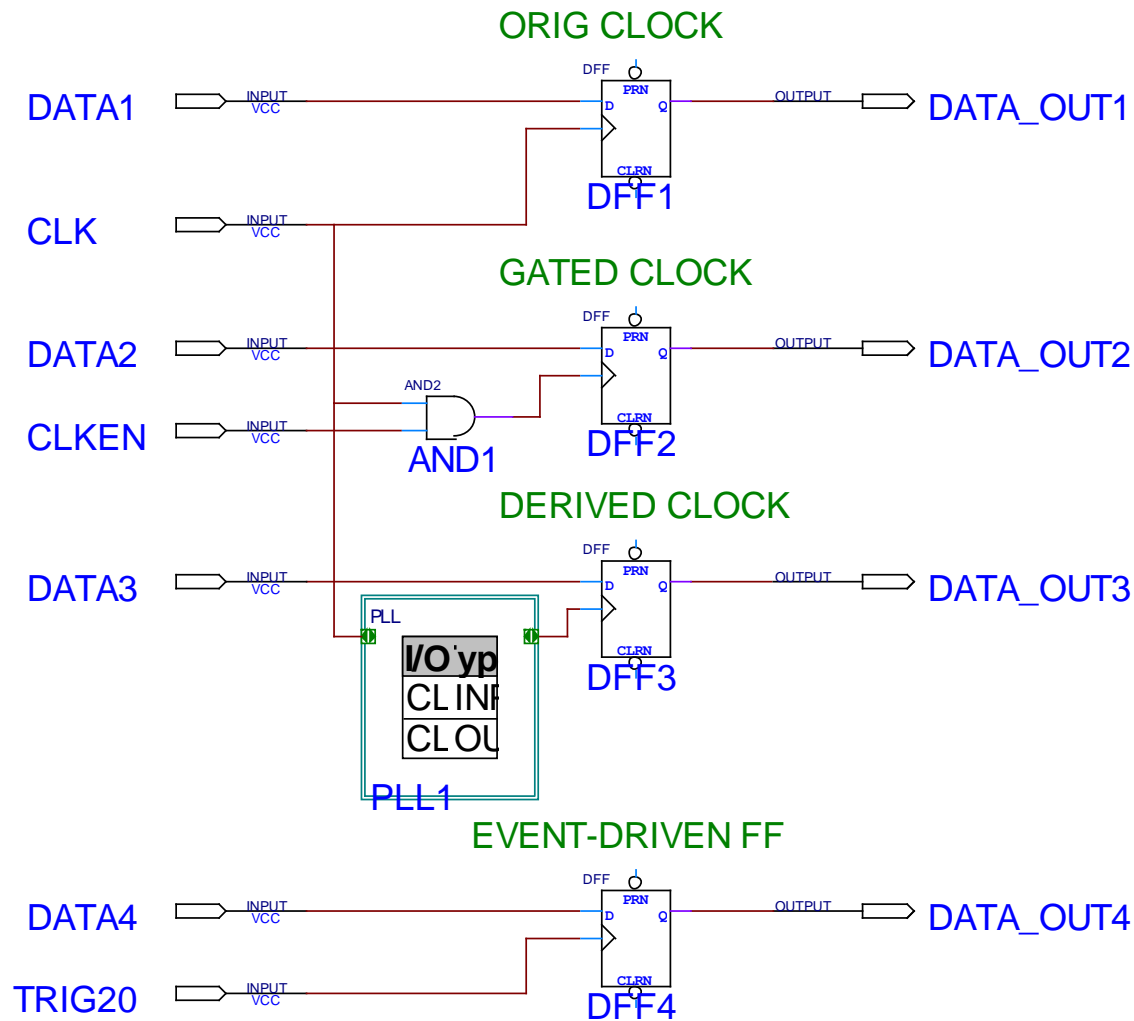

Clock Domain crossing issues

METASTABILITY

  


[Verma: Understanding clock domain crossing issues]


- › Metastability occurs when source and destination clocks edges are too close

A STEP BACK...

To 1st. Semester:

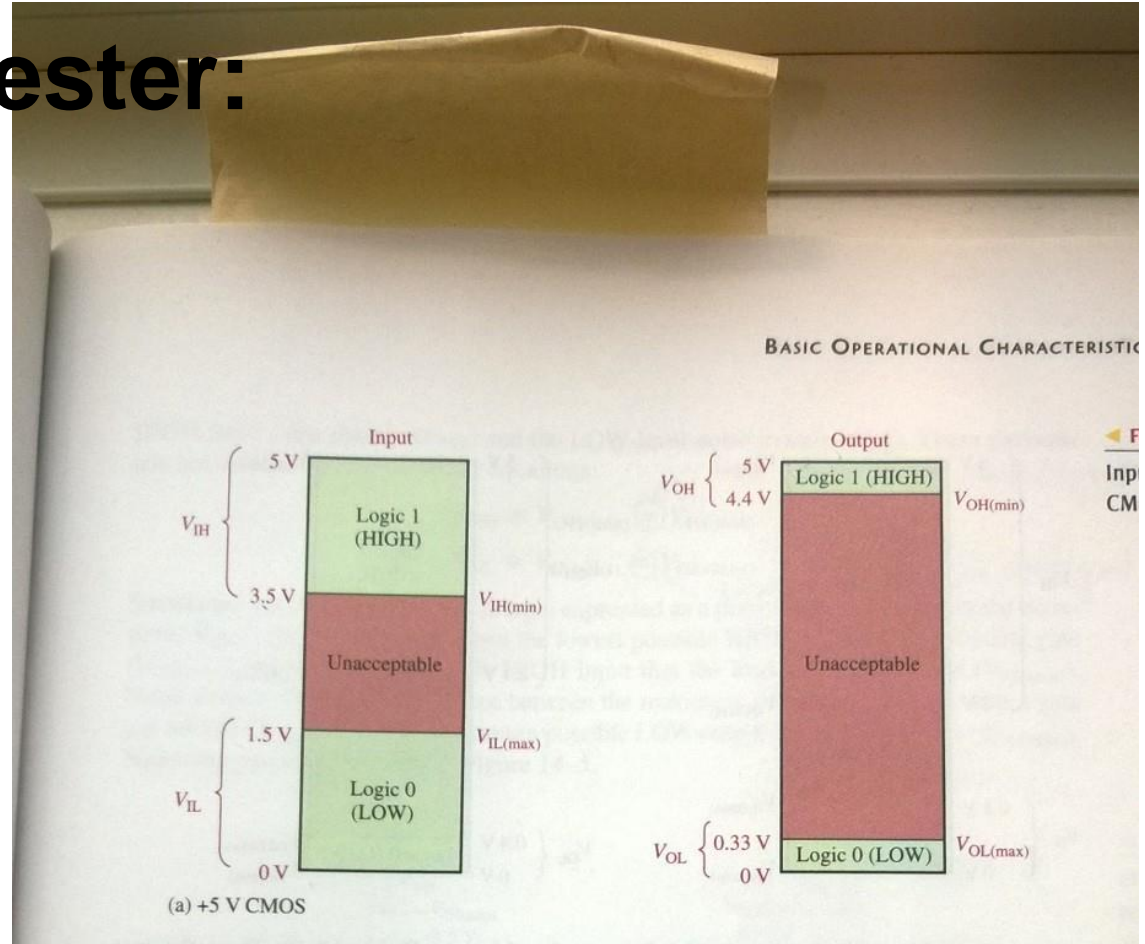


DATA LOSS

 

[Verma: Understanding clock domain crossing issues]

- › Destination Clock is too slow to capture all input signal changes

DATA COHERENCY

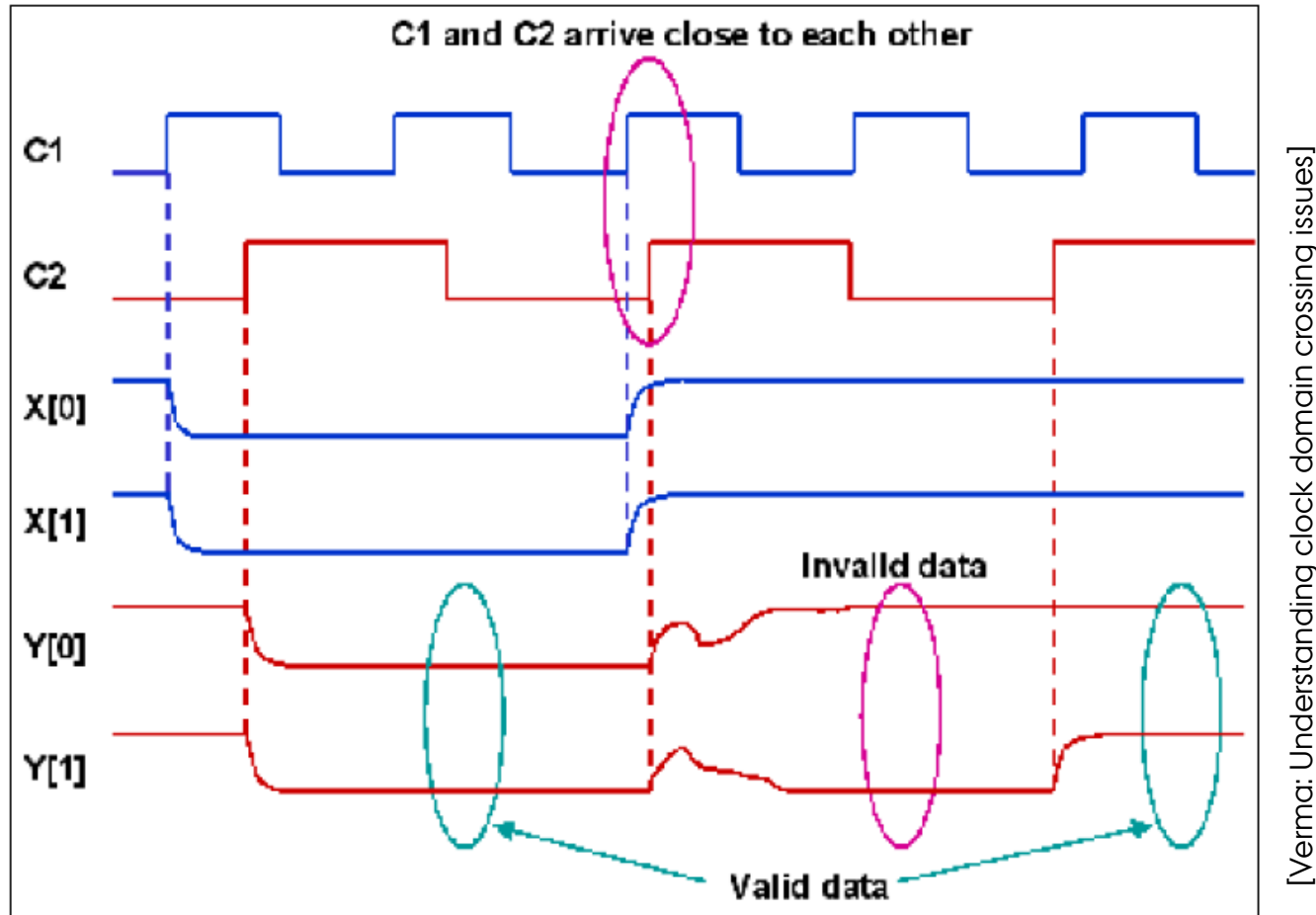

- › Data Coherency Issues: Individual bits of a bus may take different number of cycles to settle due to metastability

?

The main problem in crossing multiple clock domains is:

1. Instability
2. Metastability
3. Clock loss
4. Resampling


Solutions to Clock Domain Issues




SOLUTIONS

Clock Type	Async / Sync	Solution
Gated Clock	Synchronous, but with poorly defined phase	Avoid! Except for ASIC designs!
Derived	Synchronous, Integer or Rational multiple, well defined phase	Phase Shift / FIFO / DP MEM / FSM, double flopping
Event-Triggered	Asynchronous	Double Flopping / DP MEM / FIFO / FSM, Handshaking
Asynchronous Clocks	Asynchronous	Double Flopping / DP MEM / FIFO / FSM, Handshaking


DOUBLE FLOPPING

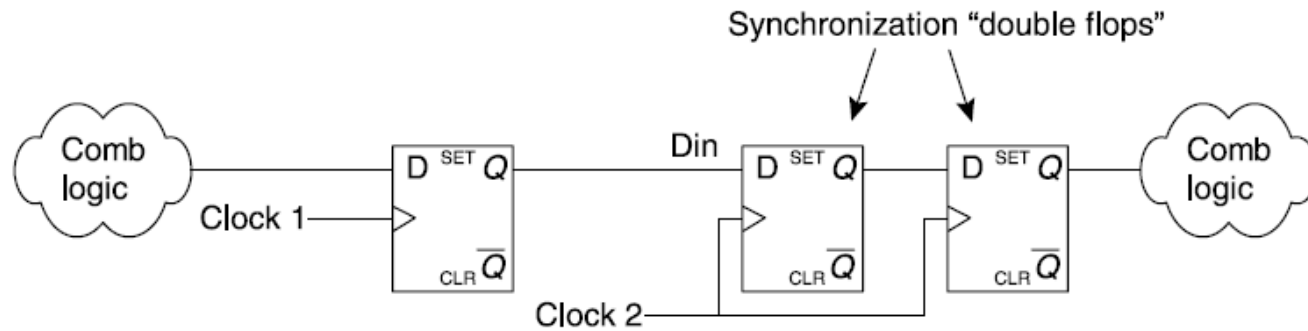

 - › Double Flopping allows the metastable signal to settle
- › Only useful for single-bit signals




FIFO / DUAL-PORT MEMORY

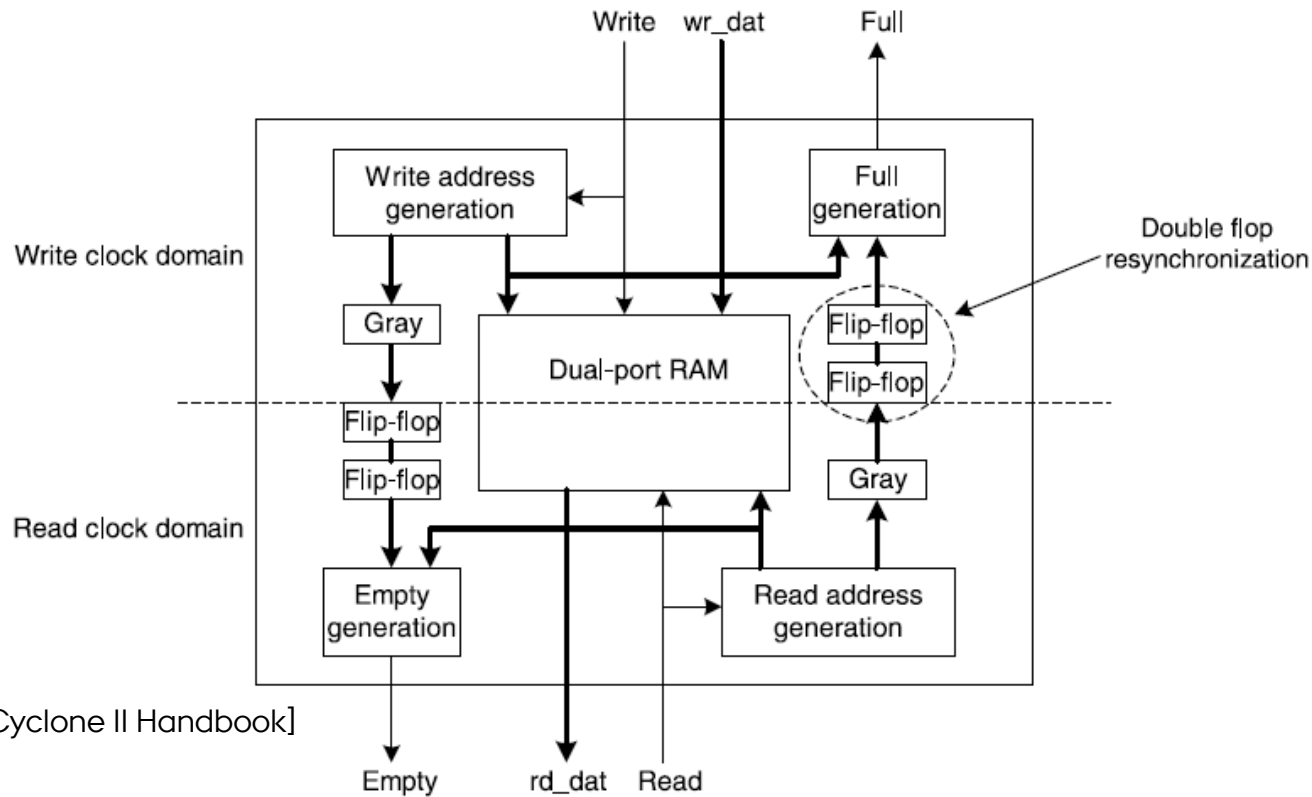

- › FIFOs and Dual-Ported Memory, is commonly used
- › Does not require external synchronization
- › System design must ensure FIFO does not overflow
- › Gray Coding used for address transfer

PUSH SYNCHRONIZER

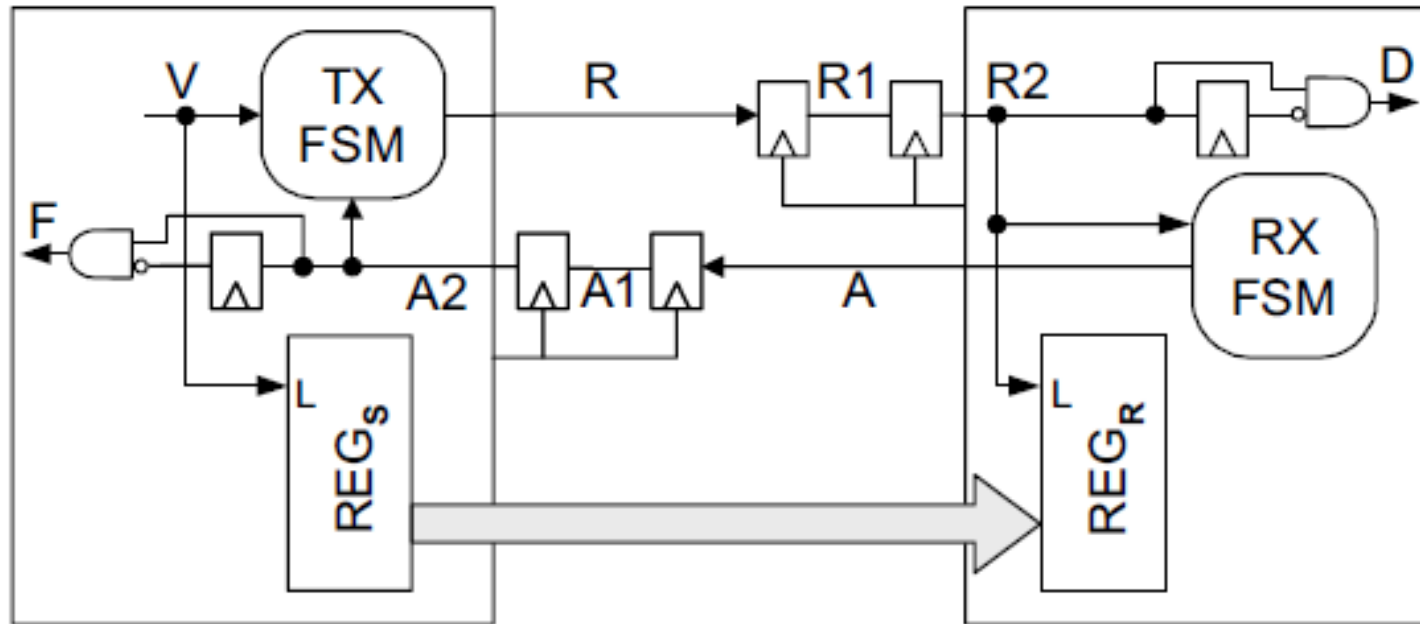

[Ran Ginosar: Fourteen Ways to Fool Your Synchronizer]

- › Example of a handshaking / FSM method for multi-bit cross-domain transfer

PUSH SYNCHRONIZER CODE

```
-- TRANSMITTER
if rising_edge(tx_clock) then
  A2 <= A1; A1 <= A;
  A3 <= A2; F <= not A3 and A2;
  case (tx_fsm_state) is
    when idle =>
      if (V = '1') then
        tx_fsm_state <= req;
        R <= '1';
      end if;
    when req =>
      if (A2 = '1') then
        tx_fsm_state <= waiting;
        R <= '0';
      end if;
    when waiting =>
      if (A2 = '0') then
        tx_fsm_state <= idle;
      end if;
    when others =>
      tx_fsm_state <= idle;
      R <= '0';
    end case;
  end if;
end if;
```


```
-- RECEIVER (input R, output A)
if rising_edge(rx_clock) then
  R2 <= R1; R1 <= R;
  R3 <= R2; D <= not R3 and R2;
  case (rx_fsm_state) is
    when idle =>
      if (R2 = '1') then
        rx_fsm_state <= ack;
        A <= '1';
      end if;
    when ack =>
      if (R2 = '0') then
        rx_fsm_state <= idle;
        A <= '0';
      end if;
    when others =>
      rx_fsm_state <= idle;
      A <= '0';
    end case;
  end if;
end if;
```

CLOCK DOMAINS SUMMARY

- › Passing signals between clock-domains is not trivial.
- › Single signals: Use double flopping
- › Multiple signals: Use FIFO / DP RAM / FSM etc.
- › If the clock phase between the clock domains is well defined, then a simple phase shift between the two may be enough
- › Going from a fast to a slow clock domain, the signal must be held stable for one destination clock cycle

Clocks in the FPGA



CLOCK DISTRIBUTION IN CYCLONE II

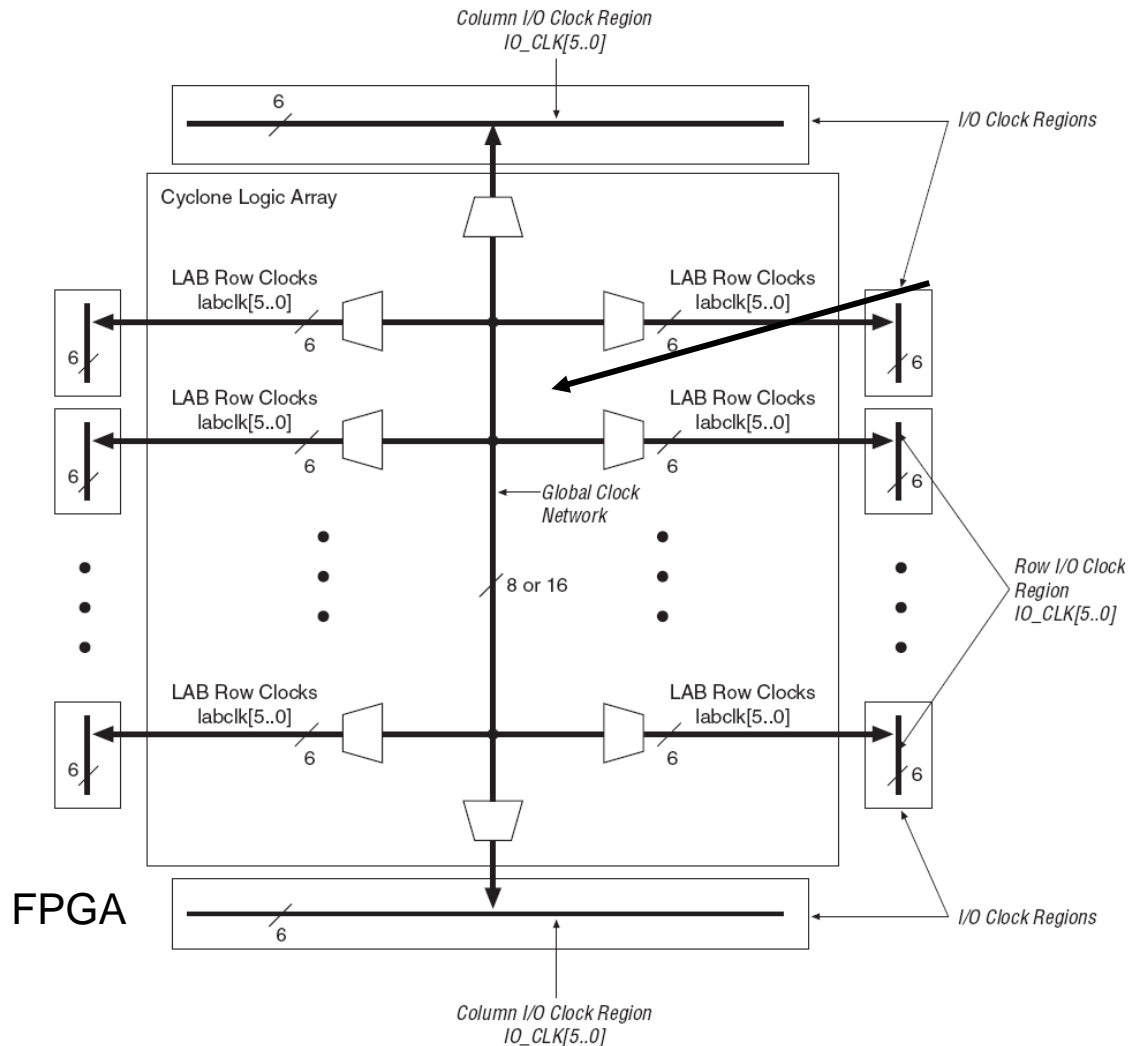

- > 8/16 Global clock nets
- > Max 6 clock nets per LAB (Logic Array Block)
- > Dedicated Clock Inputs

[Altera Corp: Cyclone II Handbook]


CLOCKS IN LOGIC- / IO ELEMENTS

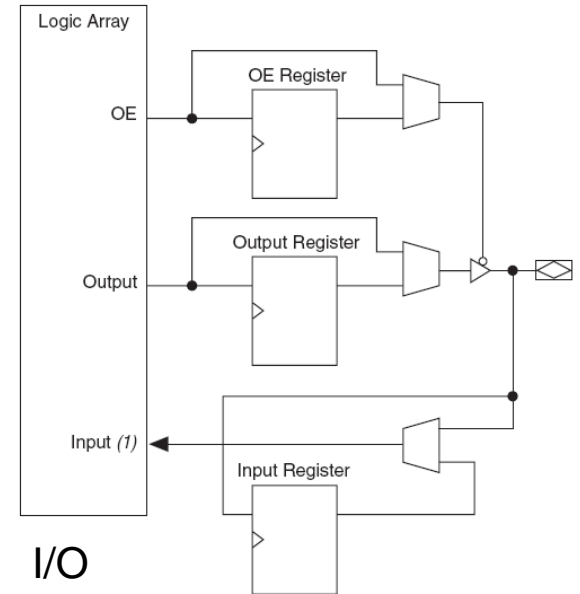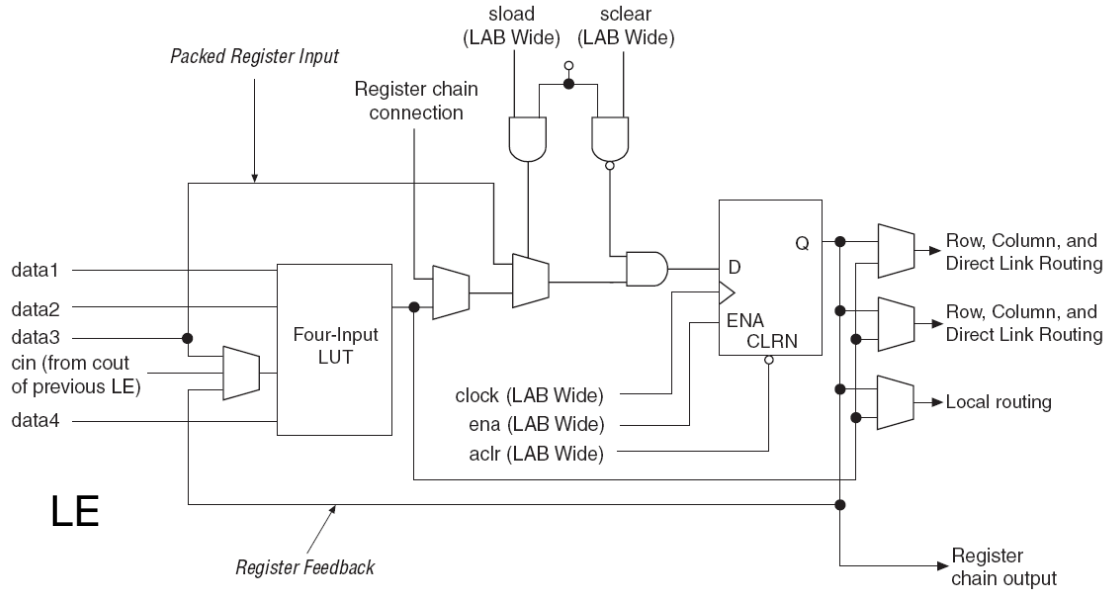

[Altera Corp: Cyclone II Handbook]

- › Clock enable per I/O cell and per LE
- › Different Input- / Output clocks allowed within an I/O cell

GATED CLOCKS (1)

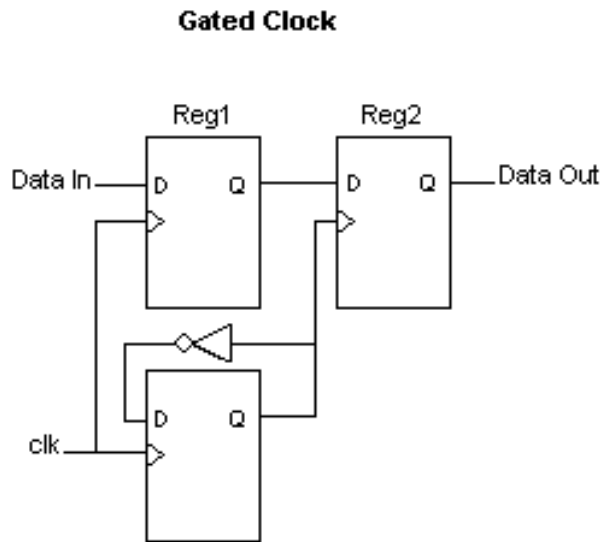


[Altera Corp: Troubleshooting
Internal Hold Violations]

```
-- Gated Clock - BAD!  
Process(clk) ...  
if rising_edge(clk) then  
    clk2 <= not clk2;  
    s1 <= DataIn;  
end if;  
  
-- Clk Enable, rising edge  
Process(clk2) ...  
if rising_edge(clk2) then  
    DataOut <= s1;  
end if;
```

Problem?

- › Gated clocks use normal inter-connect instead of global clock nets
- › Unpredictable clock phase

GATED CLOCKS (2)

 

[Altera Corp: Troubleshooting
Internal Hold Violations]


```
-- Clk Enable, rising edge
process(clk)...
if rising_edge(clk) then
  s1 <= DataIn;
  clk_en <= not clk_en;
  if clk_en = '1' then
    DataOut <= s1;
  end if;

-- Waiting for a rising edge
if rising_edge(clk) then
  event_last <= event;
  if (event = '1' and event_last = '0') then
    DataOut <= DataIn;
  end if;
end if;
```

- › Use *Clock Enable* instead of gated clocks
- › Architecture supports *Clock Enable*

PLLS I CYCLONE II

Figure 2–16. Cyclone II PLL *Note (1)*


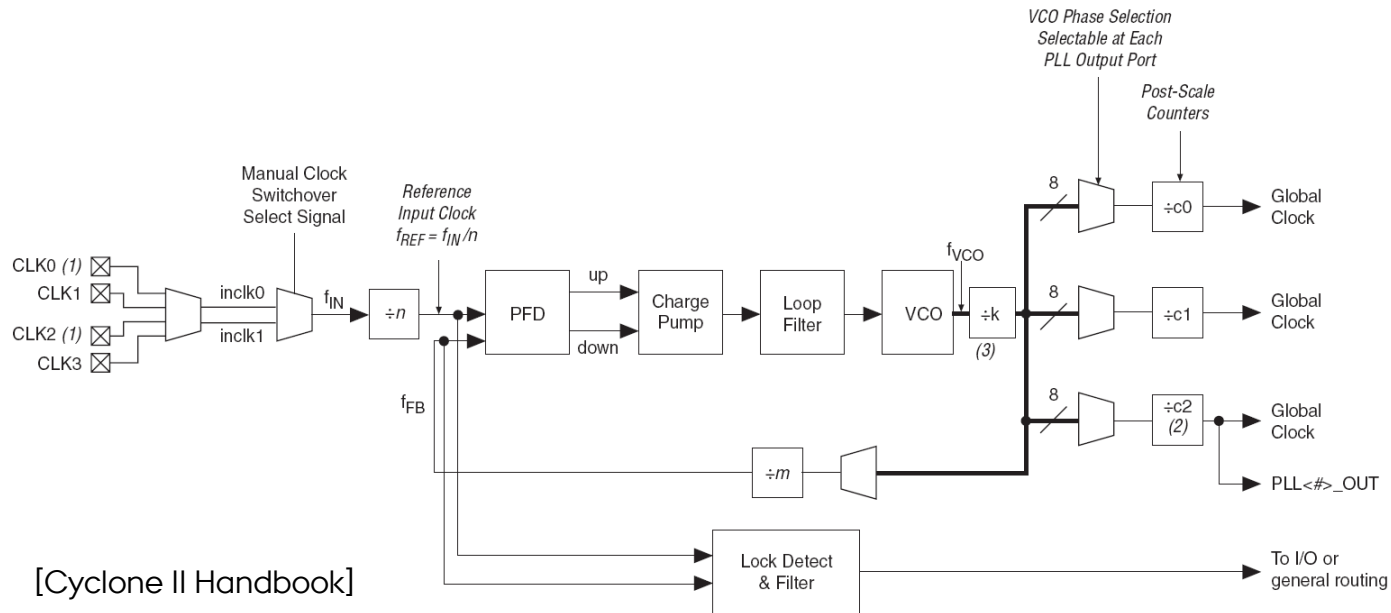


- › The PLL multiplies/divides and phase-shifts the input frequency
- › The PLL uses dedicated clock inputs
- › Output is connected to global clock nets
- › Note! Simulation Resolution > VCO frequency

CLOCKS IN AN FPGA SUMMARY



- › Only a limited number of low-skew clock nets exist
- › Avoid gated clocks in FPGAs
- › Use clock enable signals instead.
- › Supported by the architecture
- › Synchronous to the main clock
- › Use PLLs to generate derived clocks and to control the clock phase

RESETS

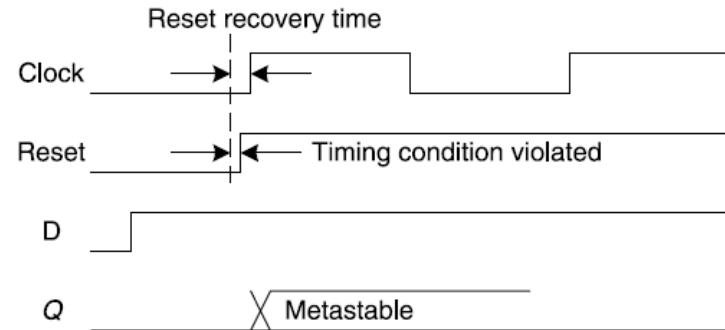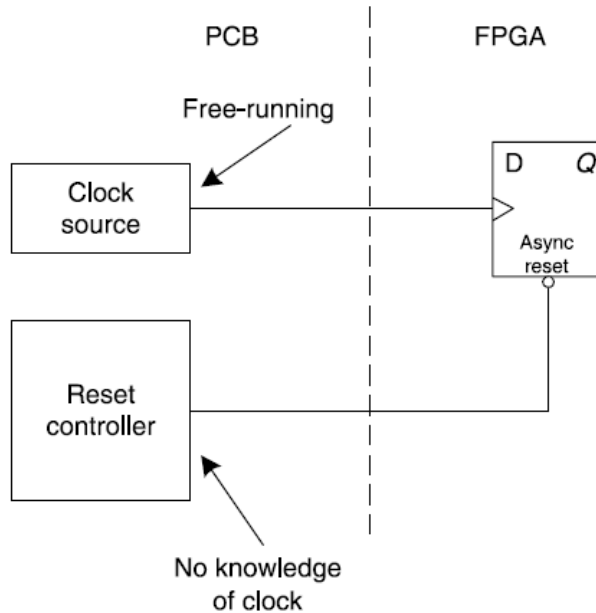


- › Asynchronous reset signals must be synchronized to their respective clocks to avoid timing violations

SYNCHRONOUS RESET

 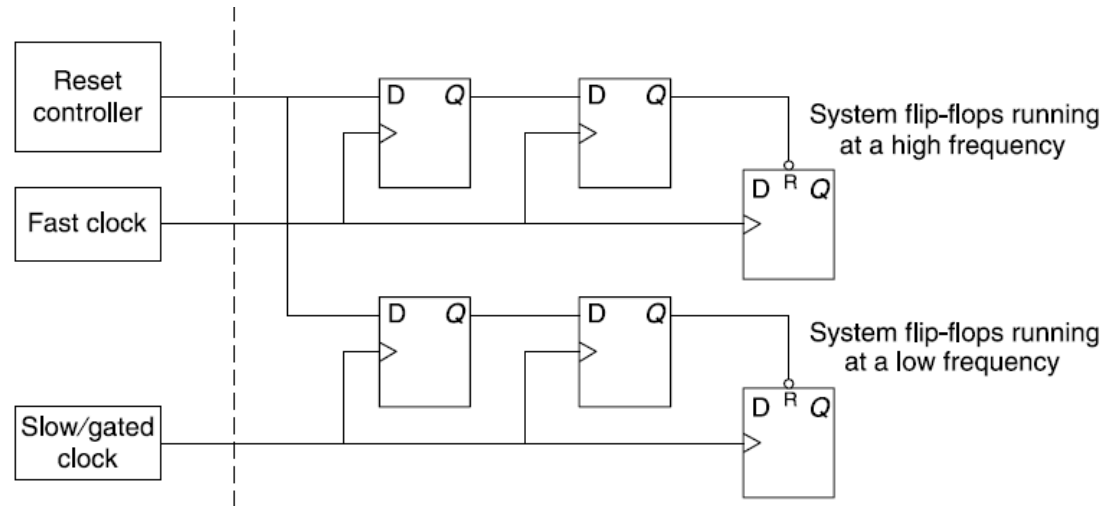

› If the reset pulse is too short, it will be missed

ASYNC- / SYNC RESET SOLUTION

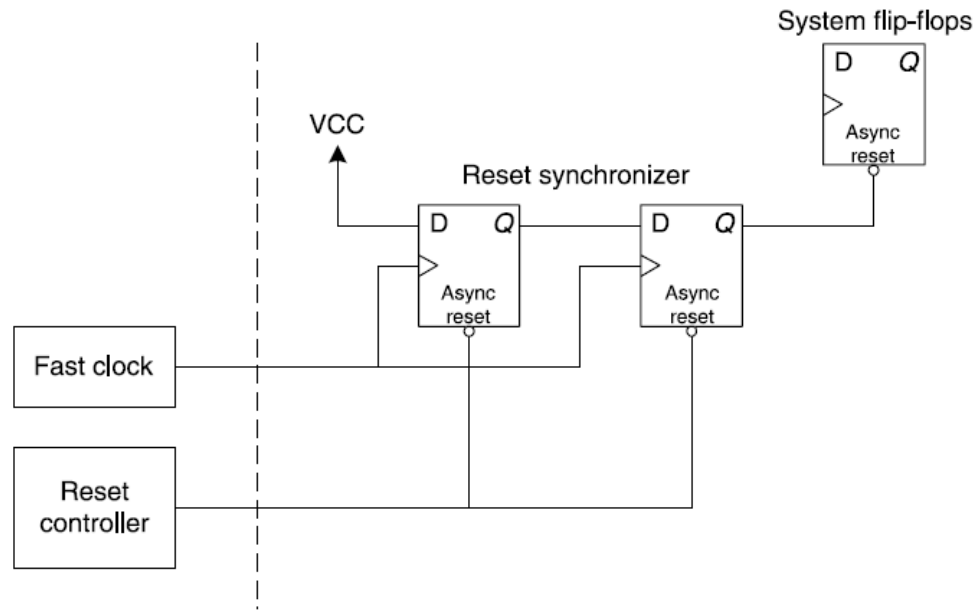

- › Suggested solution provides asynchronous assertion and synchronous de-assertion of Reset

RESETS SUMMARY

- › Asynchronous Resets must be synchronized to the clock domain where it is being used.
- › Resets must be double flopped when crossing a clock domain => One Reset per clock domain