

# CLOCK DOMAINS AND TIMING

---



# AGENDA

- › Designing for optimum speed / area
- › Optimizing for speed:
  - › Throughput, Latency, Timing
- › Optimizing for area:
  - › Memory Blocks, Reset

# OPTIMIZING FPGA DESIGNS

```
// C-Example for Pwr3  
  
XPower = 1;  
For(i=0; i < 3 ; i++)  
    XPower = X * Xpower;
```

- › How do we optimize this in terms of:
- › Speed (Throughput/Latency)?
- › Used silicium (area)?

# OPTIMIZING SPEED

- › High Throughput
  - › Data transmission and storage
  - › DSP calculations
  - › Bandwidth is important, delay less.
- › Low Latency
  - › 2-way streaming, skype, cellular phone, video conferencing
  - › Delay is crucial, bandwidth less important
  - › Latency = Propagation Delay


# WHEN/HOW TO OPTIMIZE

- › When must we optimize for speed?
  - › If throughput is too low
  - › If the system  $F_{max}$  is too low
  - › If latency is too high
  
- › What determines the solution?
  - › Increase in area allowed?
  - › Increase in latency allowed?

# ADD REGISTER LAYERS


- › Problem: Too Low Throughput
  - › Increased Latency is OK
  - › Increased Area is OK
- 
- › Break the critical timing path by introducing an extra register in the path (Introduce pipelining)

# PIPELINING

 

# ADD REGISTERS - EXAMPLE


## Original Pipeline

 

$$F_{\max} = 1/(t_{d,\text{reg}} + t_{s,\text{reg}} + t_{d,\text{comb}}) = 1/(2+20+1 \text{ ns}) = 43\text{MHz}$$

$$\text{Latency} = 2 * 1/f_{\text{clk}} + 2 \text{ ns} = 2 * 1/43\text{MHz} + 2 \text{ ns} = 48 \text{ ns}$$

## Additional Pipeline Stage Added

 


$$F_{\max} = 1/(t_{d,\text{reg}} + t_{s,\text{reg}} + t_{d,\text{comb}}) = 1/(2+10+1 \text{ ns}) = 77\text{MHz}$$


$$\text{Latency} = 3 * 1/f_{\text{clk}} + 2 \text{ ns} = 3 * 1/77\text{MHz} + 2 \text{ ns} = 41 \text{ ns}$$



# PIPELINING – EXAMPLE (1)

 

**Figure 1.1** Iterative implementation.

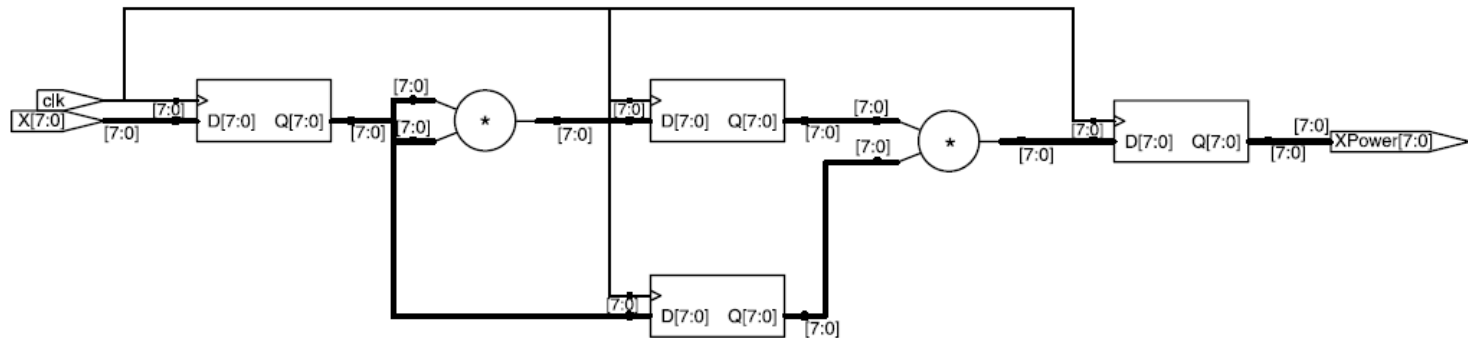

**Figure 1.2** Pipelined implementation.

# PIPELINE – EXAMPLE (2)

```
entity power3 is
  port(
    Xpower : in std_logic_vector(7 downto 0),
    clk     : in std_logic,
    X       : in std_logic_vector(7 downto 0));
end;
architecture rtl of power3 is
  signal XPower1, XPower2 : std_logic_vector(7 downto 0);
  signal X1, X2 : std_logic_vector(7 downto 0);

  proces(clk)
    if rising_edge(clk) then
      X1 <= X;
      XPower1 <= X;
      X2 <= X1;
      XPower2 <= XPower1 * X1;
      XPower <= XPower2 * X2;
    end process;
end rtl;
```

# PARALLELIZE STRUCTURE

- › Problem: Too Low Throughput/High Latency


- › Increased Latency is NOT OK.

- › Increased Area is OK

- › Split the design into several parallel tasks (more processes)

# PARALLELIZE - EXAMPLE


## Original Pipeline

 

$$F_{\max} = 1/(td,reg + ts,reg + td,comb) = 1/(2+10+1\text{ ns}) = 77\text{ MHz}$$

$$\text{Latency} = 3 * 1/f_{\text{clk}} + 2\text{ ns} = 3 * 1/77\text{ MHz} + 2\text{ ns} = 41\text{ ns}$$

## Parallelized Structure

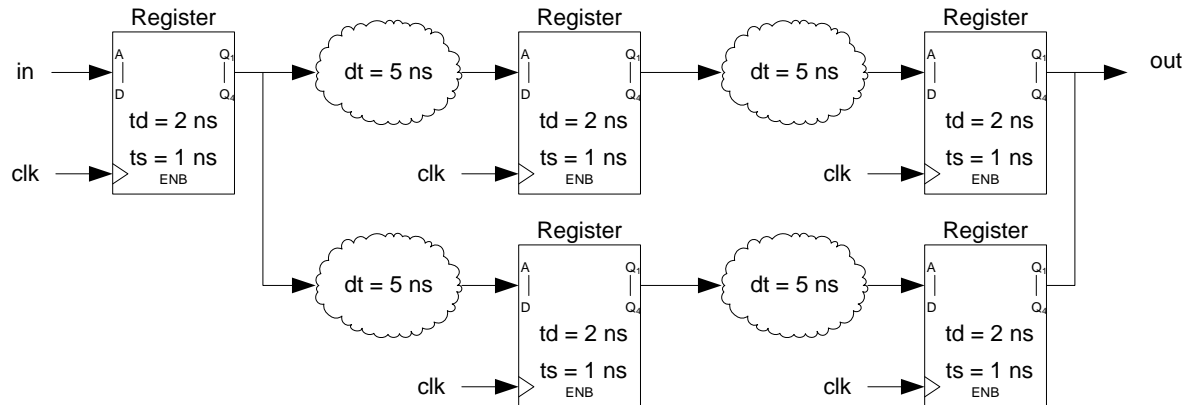

$$F_{\max} = 1/(td,reg + ts,reg + td,comb) = 1/(2+5+1\text{ ns}) = 125\text{ MHz}$$

$$\text{Latency} = 3 * 1/f_{\text{clk}} + 2\text{ ns} = 3 * 1/125\text{ MHz} + 2\text{ ns} = 26\text{ ns}$$

# FLATTEN STRUCTURE

- › Problem: Too Low Throughput/High Latency
  - › Increased Latency is NOT OK
  - › Increased Area is NOT OK
- › Remove un-intentional priorities in the design (typically "if-else" statements, replace these by "case" statements)

# FLATTEN STRUCTURE – EXAMPLE (1)

## Prioritized

```
if input = "0001" then
    OutA <= '1';
elsif input = "0010" then
    OutB <= '1';
elsif input = "0100" then
    OutC <= '1';
else
    OutF <= '1';
end if;
```


## Not Prioritized

```
case input is
    when "0001" =>
        OutA <= '1';
    when "0010" =>
        OutB <= '1';
    when "0100" =>
        OutC <= '1';
    when others =>
        OutF <= '1';
end case;
```


- › Priority adds combinatorial logic to the signal delay path
- › "Case" sentence is implemented as a simple mux

# FLATTEN STRUCTURE – EXAMPLE (2)

**Prioritized  
(if)**

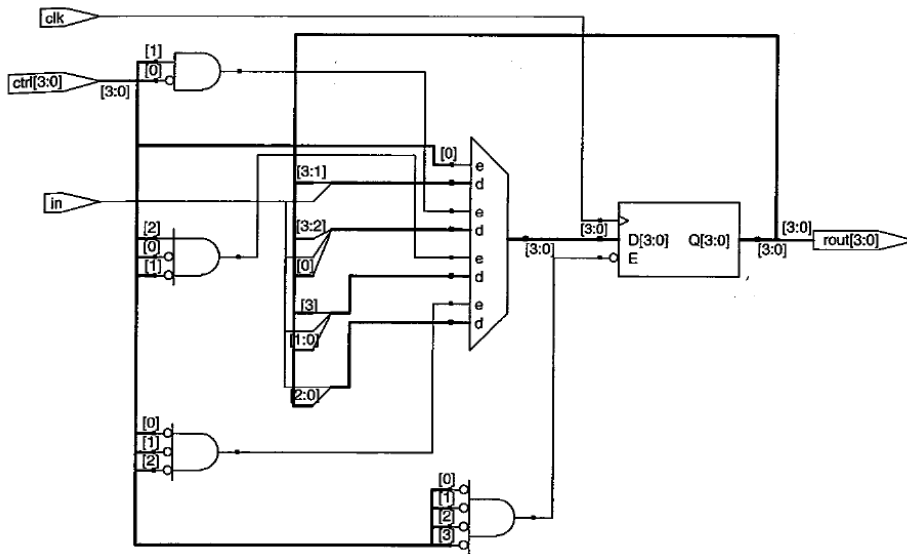

**Not Prioritized  
(case)**

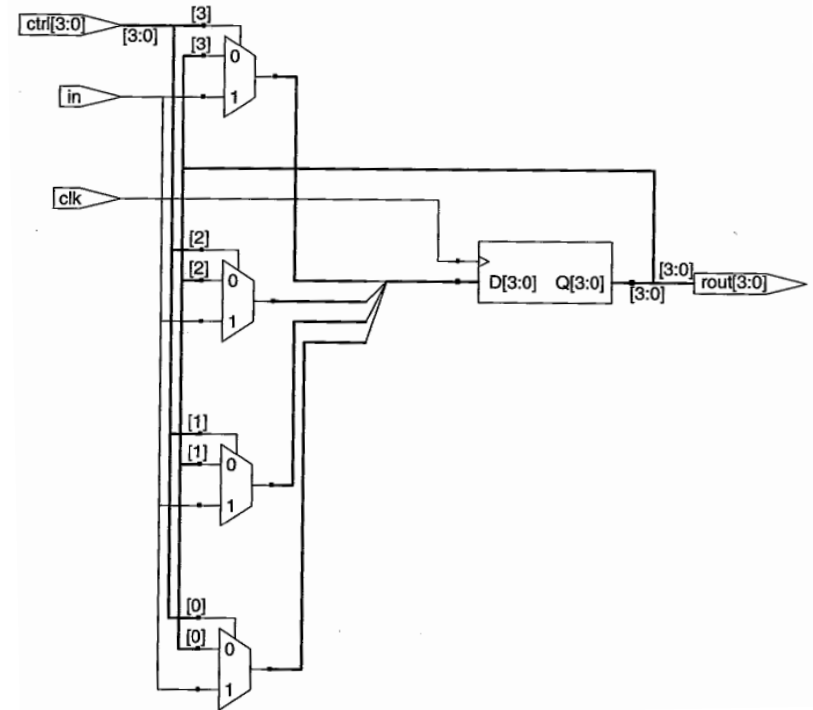


# REGISTER BALANCING

- › Problem: Too Low Throughput/High Latency
  - › Increased Latency is NOT OK
  - › Increased Area is NOT OK
- › The  $F_{max}$  of a pipelined design is constrained by the longest combinatorial delay in the pipeline.
- › By distributing the the combinatorial logic evenly into each step of the pipeline,  $F_{max}$  is maximized



# REGISTER BALANCING - EXAMPLE


## Original Pipeline

 

$$F_{\max} = 1/(td,reg + ts,reg + td,comb,max) = 1/(2+1+10\text{ ns}) = 77\text{ MHz}$$

$$\text{Latency} = 3 * 1/f_{\text{clk}} + (2+7)\text{ns} = 3 * 1/77\text{MHz} + 12\text{ ns} = 48\text{ ns}$$

## Balanced Pipeline

 


$$F_{\max} = 1/(td,reg + ts,reg + td,comb) = 1/(2+6+1\text{ ns}) = 111\text{ MHz}$$

$$\text{Latency} = 3 * 1/f_{\text{clk}} + (2+6)\text{ns} = 3 * 1/111\text{MHz} + 8\text{ ns} = 35\text{ ns}$$


# PATH RE-ORDERING

- › Problem: Too Low Throughput/High Latency
  - › Increased Latency is NOT OK
  - › Increased Area is NOT OK
- › The combinatorial delay path may be shortened, by decreasing the number of series elements in the combinatorial chain from source to drain.

# PATH RE-ORDERING - EXAMPLE

 

**Figure 1.11** Long critical path.

 

**Figure 1.12** Logic reordered to reduce critical path.

# PATH RE-ORDERING EXAMPLE

## Original

```
module randomlogic(  
  output reg [7:0] Out,  
  input      [7:0] A, B, C,  
  input      clk,  
  input      Cond1, Cond2);  
always @(posedge clk)  
  if(Cond1)  
    Out <= A;  
  else if(Cond2 && (C < 8))  
    Out <= B;  
  else  
    Out <= C;  
endmodule
```

## Re-Ordered

```
module randomlogic(  
  output reg [7:0] Out,  
  input      [7:0] A, B, C,  
  input      clk,  
  input      Cond1, Cond2);  
wire CondB = (Cond2 & !Cond1);  
always @(posedge clk)  
  if(CondB && (C < 8))  
    Out <= B;  
  else if(Cond1)  
    Out <= A;  
  else  
    Out <= C;  
endmodule
```


**Translate to VHDL...**

# REDUCE LATENCY

- › Problem: Too High Latency
  - › Increased Latency is NOT OK
  - › Increased Area is OK
  - › Reduced Throughput is OK
- 
- › Implement functionality in combinatorial logic to remove pipelining

# REDUCE LATENCY - EXAMPLE


## Pipelined Design

 

$$F_{\max} = 1/(t_{d,\text{reg}} + t_{s,\text{reg}} + t_{d,\text{comb}}) = 1/(2 + 10 + 1 \text{ ns}) = 77\text{MHz}$$

$$\text{Latency} = 3 * 1/f_{\text{clk}} + (2 + 10)\text{ns} = 3 * 1/77\text{MHz} + 12 \text{ ns} = 51 \text{ ns}$$

## De-Pipelined Design for low latency

 

$$F_{\max} = 1/(t_{d,\text{reg}} + t_{s,\text{reg}} + t_{d,\text{comb}}) = 1/(23 \text{ ns}) = 43\text{MHz}$$

$$\text{Latency} = 1 * 1/f_{\text{clk}} + 22\text{ns} = 1 * 1/43\text{MHz} + 22 \text{ ns} = 46 \text{ ns}$$

# OPTIMIZING SPEED SUMMARY

*When a higher throughput is needed:*

- › Add registers – Pipeline the design

*When Lower Latency is needed:*

- › Don't pipeline, use combinatorial logic

*When a higher Throughput is needed, but area and latency must be maintained:*

- › Parallel structure – Split design in to parallel tasks
- › Flatten Design – Remove unintentional priorities
- › Register Balancing – Distribute combinatorial elements evenly in the pipeline.
- › Path Re-Ordering – Shorten the critical timing path

# Optimizing Area



# OPTIMIZING AREA

- › Several resources can be the limiting factor in an FPGA design:
  - › Logical elements
  - › Registers
  - › Memory
  - › Routing Resources (LAB interconnect)
  - › Clocks


# STRATEGIES FOR REDUCING AREA

- › Reducing LE count:
- › Rolling up the pipeline
- › Resource sharing among functions
- › Choosing the right reset strategy
- › Using memory blocks
- › Improving Routing
- › Use a synchronous design
- › Think “dataflow” when designing
- › Reducing Clock Count
- › Use few clocks, but a lot of *clock enable* signals

# ROLL-UP PIPELINE


- › Opposite to unrolling the pipeline
- › Look into how more cycles can produce less logic
- › Example: Multiplier
- › Pipelined: 1-cycles, ~ 10 LE
- › Multiplexed: 8-cycles, ~ 3 LE

# CONTROL BASED LOGIC SHARING

 

- › Using one multiplier per tap allows the filter to run at  $>200\text{MHz}$
- › If the throughput frequency required is lower, then the multiplier could be reused.
- › Requires additional control logic

# RESOURCE SHARING

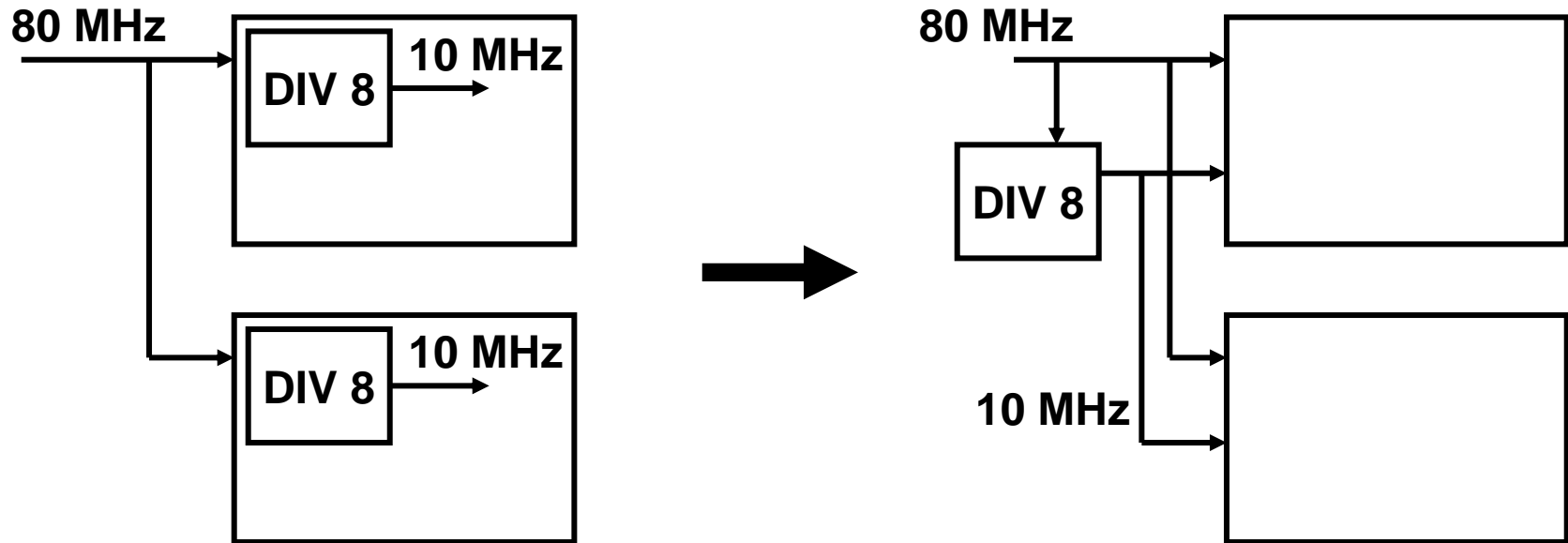

- › Local instances of a similar signal can be replaced by a “global” top-level signal.
- › Thus reducing identical logic
- › May not be detected automatically by the compiler

# RESET STRATEGY

- › Using reset for resources that does not have a build-in reset, will increase area consumption
- › Using asynchronous reset for resources with synchronous reset will also increase area consumption

# ASYNC / SYNC RESETS


## Asynchronous Reset

```
If reset = 0 then
    sr <= 0;
Elsif rising_edge(clk) then
    sr <= shift_right(iDat, 1);
Endif;
```


## Synchronous Reset

```
if rising_edge(clk) then
    if reset = 0 then
        sr <= 0;
    else
        sr <= shift_right(iDat, 1);
    endif;
Endif;
```

# RESET OF RESOURCE WITH NO RESET

 

**Figure 2.5** Shift register implemented with SRL16 element.

 

**Figure 2.6** Shift register implemented with flip-flops.

- › To use build-in functions
- › Check if they have build in reset
- › Consider if reset is necessary
- › Check technology map viewer



# RESOURCE WITH SYNC RESET (1)

- › DSP Blocks have build-in sync reset inputs
- › Using **async** reset adds logic to outputs
- › Check blocks before adding reset signals

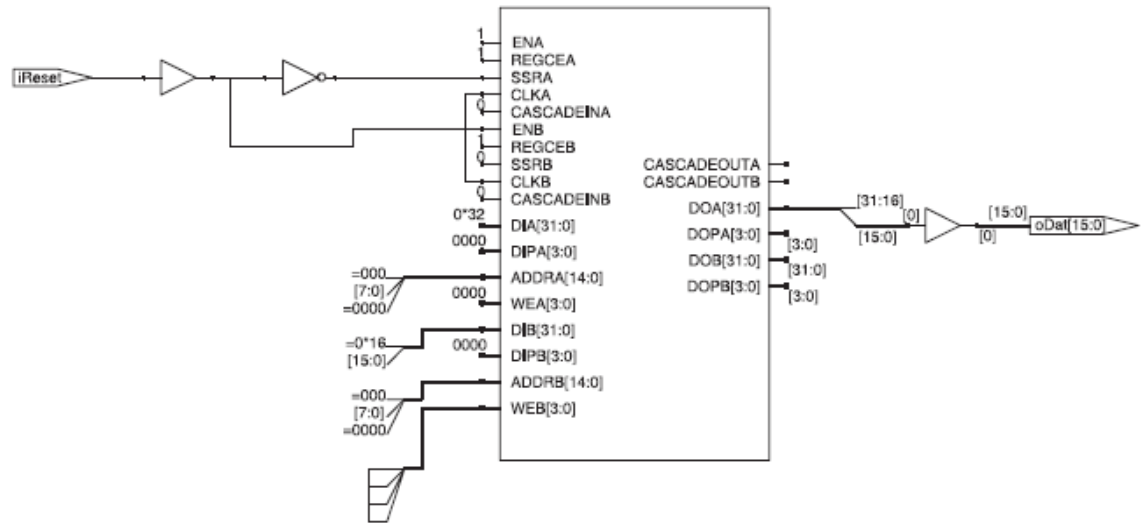


Figure 2.9 Xilinx BRAM with synchronous reset.

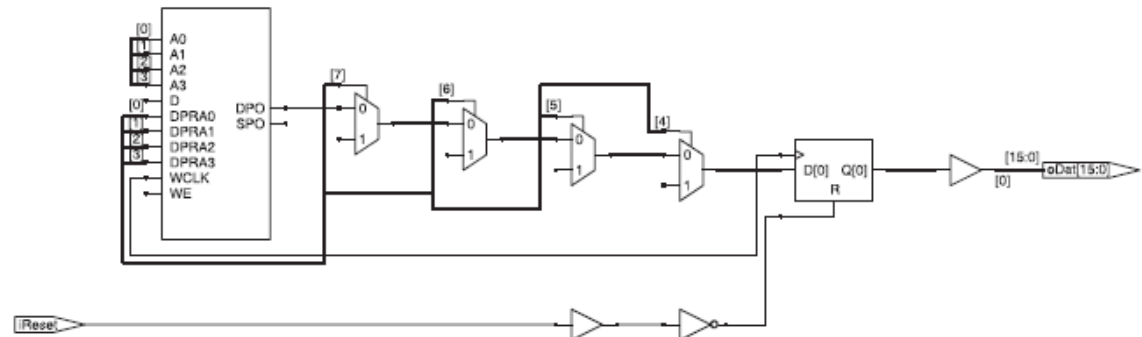


Figure 2.10 Xilinx BRAM with asynchronous reset logic.

# RESOURCE WITH SYNC RESET (2)

**Table 2.4** Resource Utilization for BRAM with Synchronous and Asynchronous Resets

Implementation	Slices slice	Flip-flops	4 Input LUTs	BRAMs
Asynchronous reset	3415	4112	2388	0
Synchronous reset	0	0	0	1

› DON'T USE ASYNC RESET TO RESET RAM!!!

# USE THE RIGHT CODING STYLE

```
ARCHITECTURE arch OF shift_1x64 IS
TYPE sr_length IS ARRAY (63 DOWNT0 0) OF STD_LOGIC;
SIGNAL sr: sr_length;
BEGIN
PROCESS (clk)
BEGIN
IF (clk'EVENT and clk = '1') THEN
IF (shift = '1') THEN
sr(63 DOWNT0 1) <= sr(62 DOWNT0 0);
sr(0) <= sr_in;
END IF;
END IF;
END PROCESS;
sr_out <= sr(63);
END arch;
```

- › Altera Recommended HDL Coding Style:
- › [http://www.altera.com/literature/hb/qts/qts\\_qii51007.pdf](http://www.altera.com/literature/hb/qts/qts_qii51007.pdf)



# USING MEMORY

- › Compiler tries to implement registers in RAM where feasible
- › Avoid large arrays of `std_logic_vector` = Matrix in registers => use Memory blocks instead
- › Slow state machines may use time-multiplexing with coefficients stored in memory

# OPTIMIZING AREA SUMMARY

- › If you can allow more clock cycles, use time-division to re-use logic
- › Consider using fewer central counters instead of multiple spread around the design hierarchy
- › Be careful when choosing the reset strategy
- › If resource does not support reset, then function will be implemented with std logic elements instead of dedicated hardware → More logic!
- › Async reset of resource with sync reset only adds logic to outputs. RAM example!
- › Use memory block when feasible